



TOP, here's the master wiring diagram for a 1967 sedan (thanks to Robert Bentley Publishers). It's a great guide that will help you tackle this tricky job. ABOVE, a look at the finished wiring job, and the ten-fuse panel used on the '67 Bug. Fuse panel shows modified wiring method used for fused park light application (park lights will remain lit when headlights are on). ABOVE RIGHT, this is what Morley's car looks like after we completed our rewiring. Clean, neat, color-coded and ready for years of use.